

# Diodes for Signal Processing

EE122

D. W. Parent

# Diodes can be used for more than just rectification.

- Light emitting diodes
- Laser diodes
- Solar Cells
- Signal Processing


$$I = I_s \times \left( e^{\frac{V}{\eta V_T}} - 1 \right)$$

This is a lot of floating point operations.  
I count 17!

$$e^x = 1 + x + \frac{x^2}{2} + \frac{x^3}{6} + \frac{x^4}{24} \dots$$
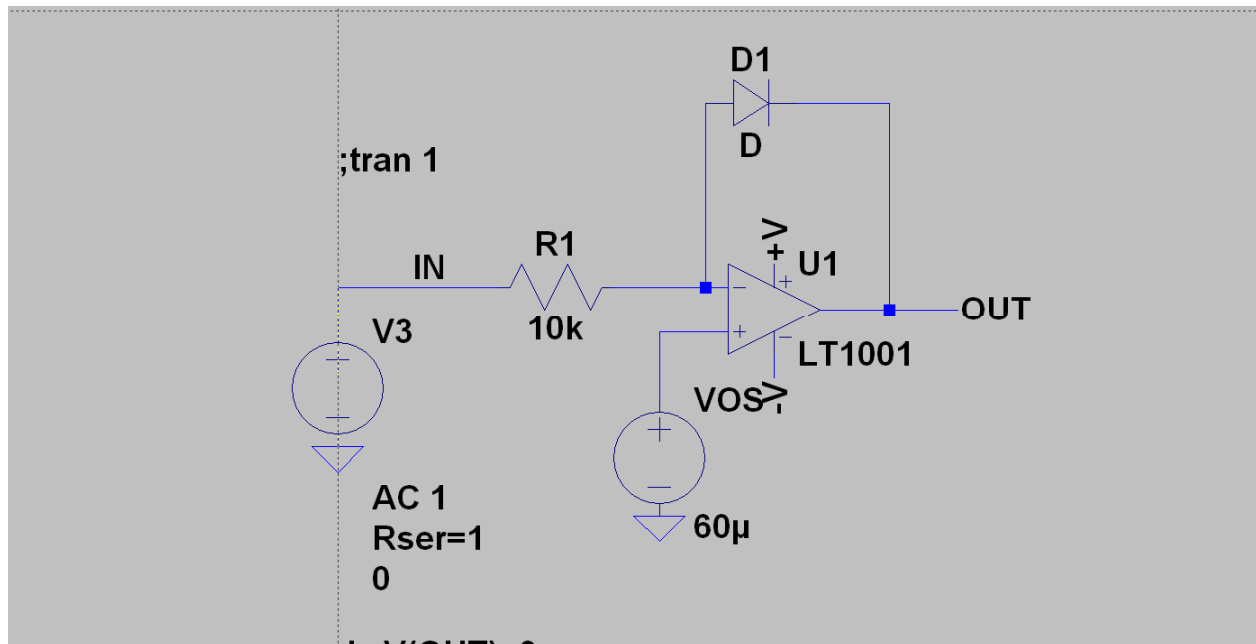
# Log amplifier

$$V_{out} = -V_T \ln\left(\frac{V_{in}}{I_s R}\right)$$



# There are 4 DC spice parameters for a diode

IS Saturation current (Given in Amps)

N Emission Coefficient (No Units)

RS Parasitic resistance (Given in  $\Omega$ )

BV Breakdown Voltage (Given in Volts)

IBV Breakdown Current (Given in Amps)

GMIN is a small resistance

To prevent a value of zero current from flowing. Usually set to  $10^{-12}S$

$$I_s := 1 \times 10^{-7}$$

$$n := 2$$

$$r_s := 100$$

$$V_t := .0259$$


$$BV := 10$$

$$G_{\min} := 1 \times 10^{-9}$$


$$IBV := I_s \cdot \frac{BV}{V_t}$$

$$I_{D0_i} := \begin{cases} \left[ I_s \cdot \left( e^{\frac{V_{D0_i}}{n \cdot V_t}} - 1 \right) + V_{D0_i} \cdot G_{\min} \right] & \text{if } V_{D0_i} > -BV \\ (-IBV) & \text{if } V_{D0_i} = -BV \\ \left[ -I_s \cdot \left[ e^{\frac{-(BV + V_{D0_i})}{V_t}} - 1 + \frac{BV}{V_t} \right] \right] & \text{if } V_{D0_i} < -BV \end{cases}$$

# Full Diode Response

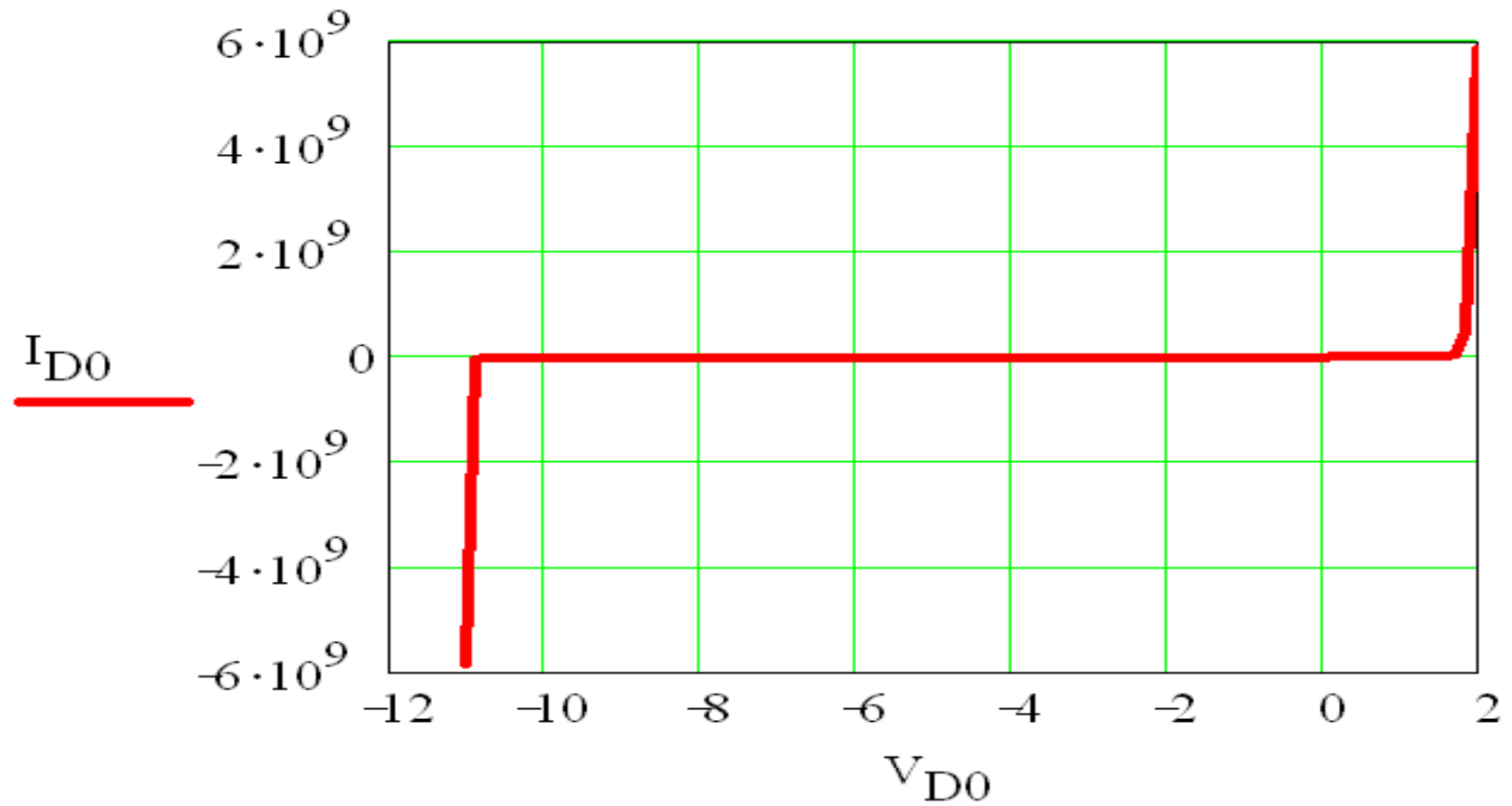


# Test the diode of a NMOS

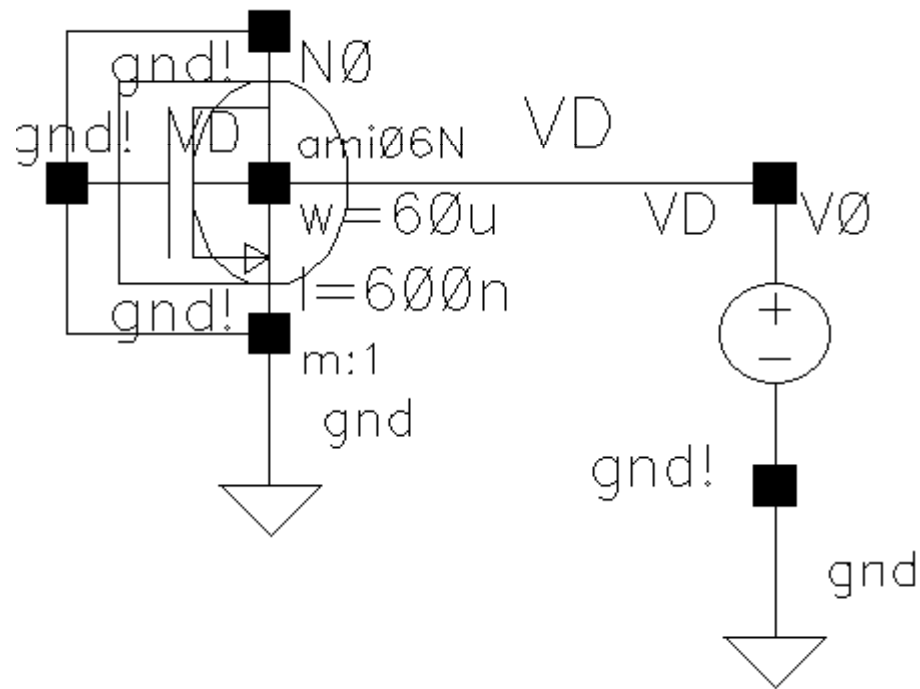


Note there are two diodes being tested.

# Forward Bias Diode Linear

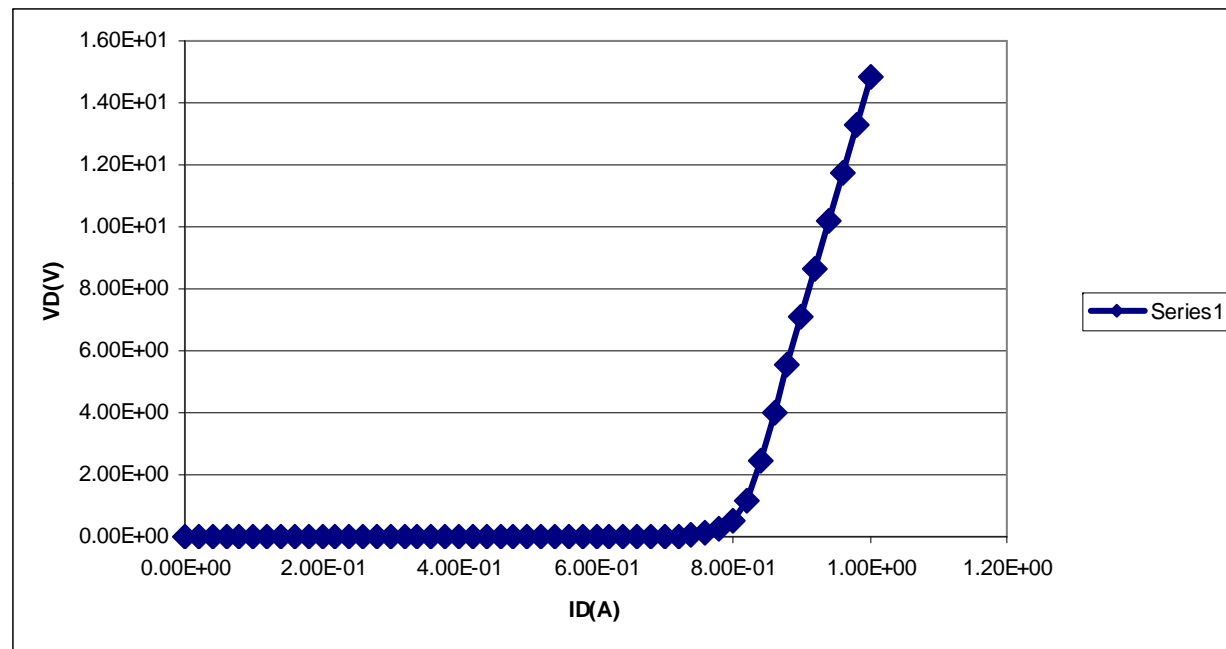

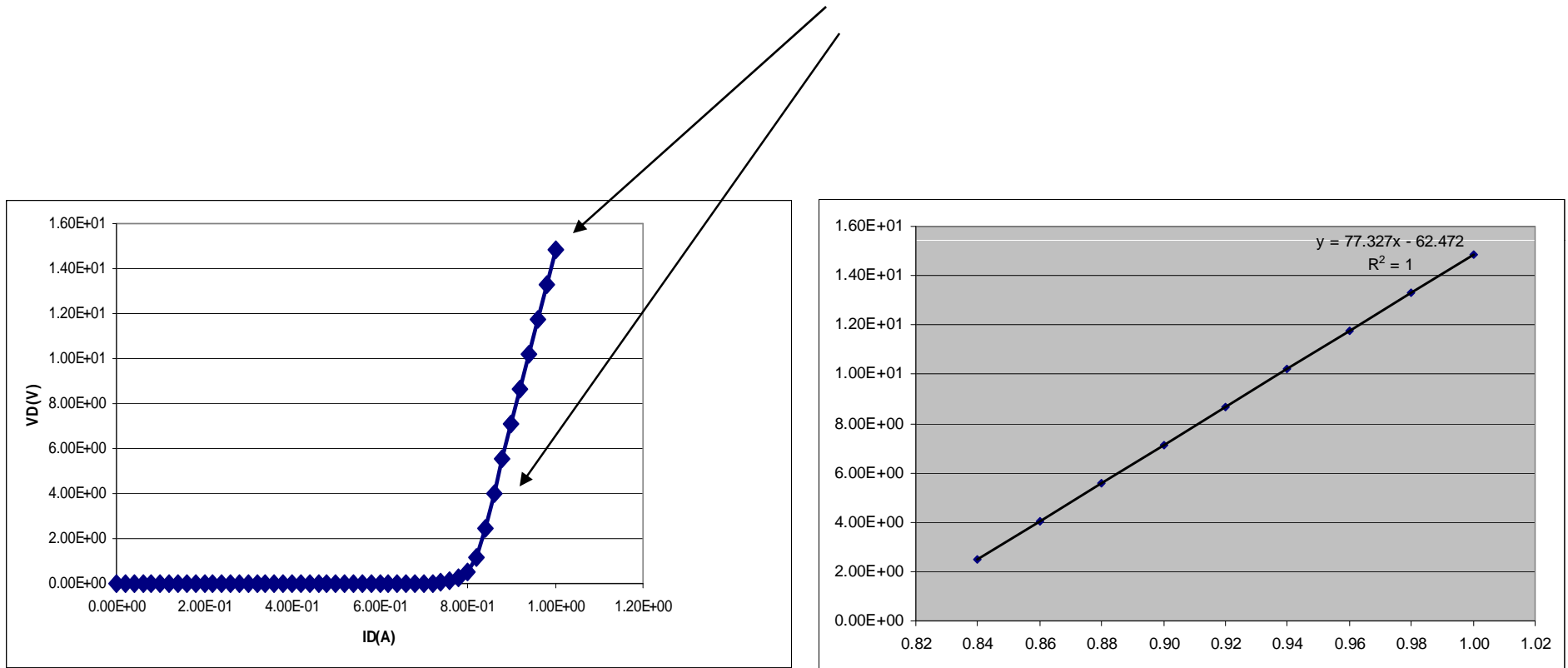
# Take the RS value from the Linear part of the diode curve





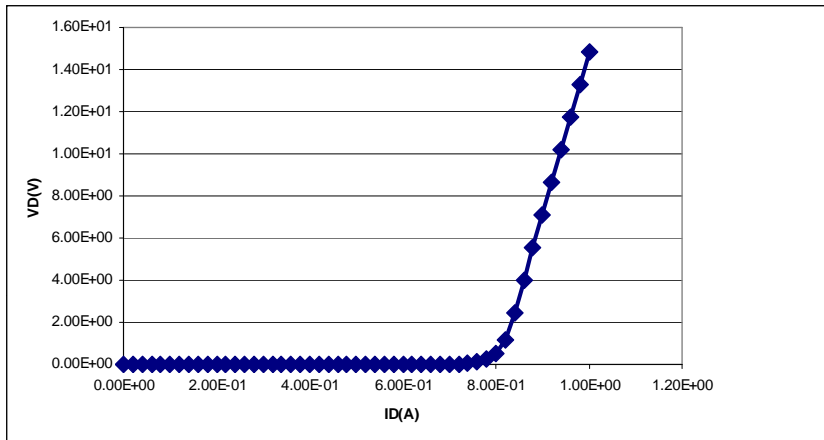
# Forward Bias Ln Scale (RS position omitted)




$$I_S := e^{-31.543} \quad I_S = 2 \times 10^{-14}$$
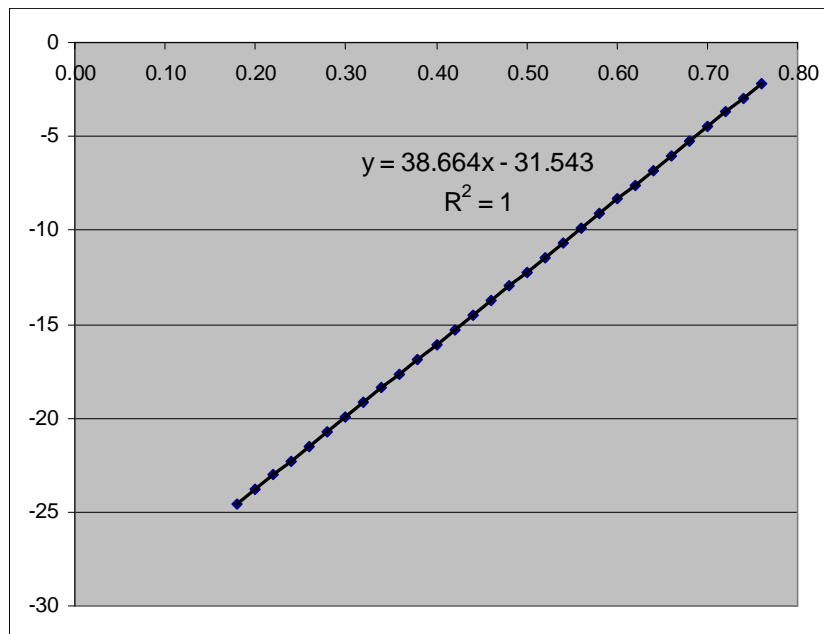
$$n := \frac{1}{38.664 \cdot 0.0259} \quad n = 0.999$$




Do not use linear  
Region of Diode  
Or too close to 0V.  
The RS value and GMIN  
Will skew the results.
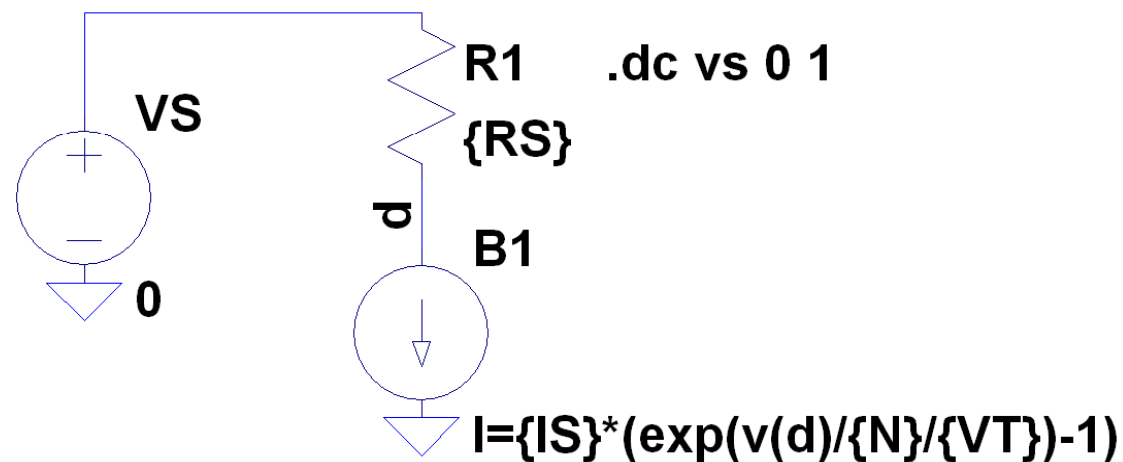
# Behavioral DC models are easy to create.




```
.param N=1  
.param IS=1e-9  
.param VT=.0259  
.param RS=1
```
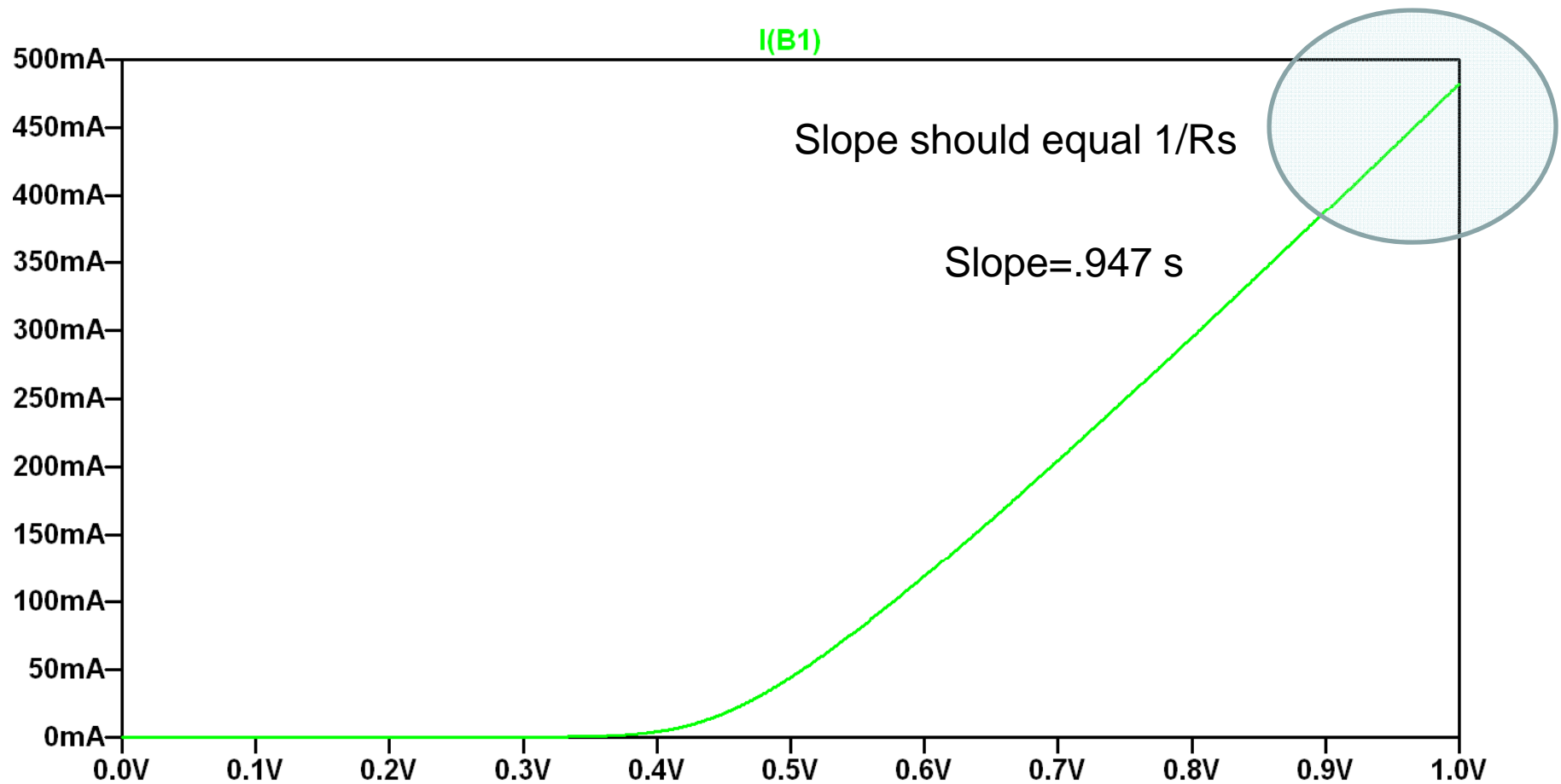
# Series Resistance Dominates at higher voltages.




# To see exponential function plot log.

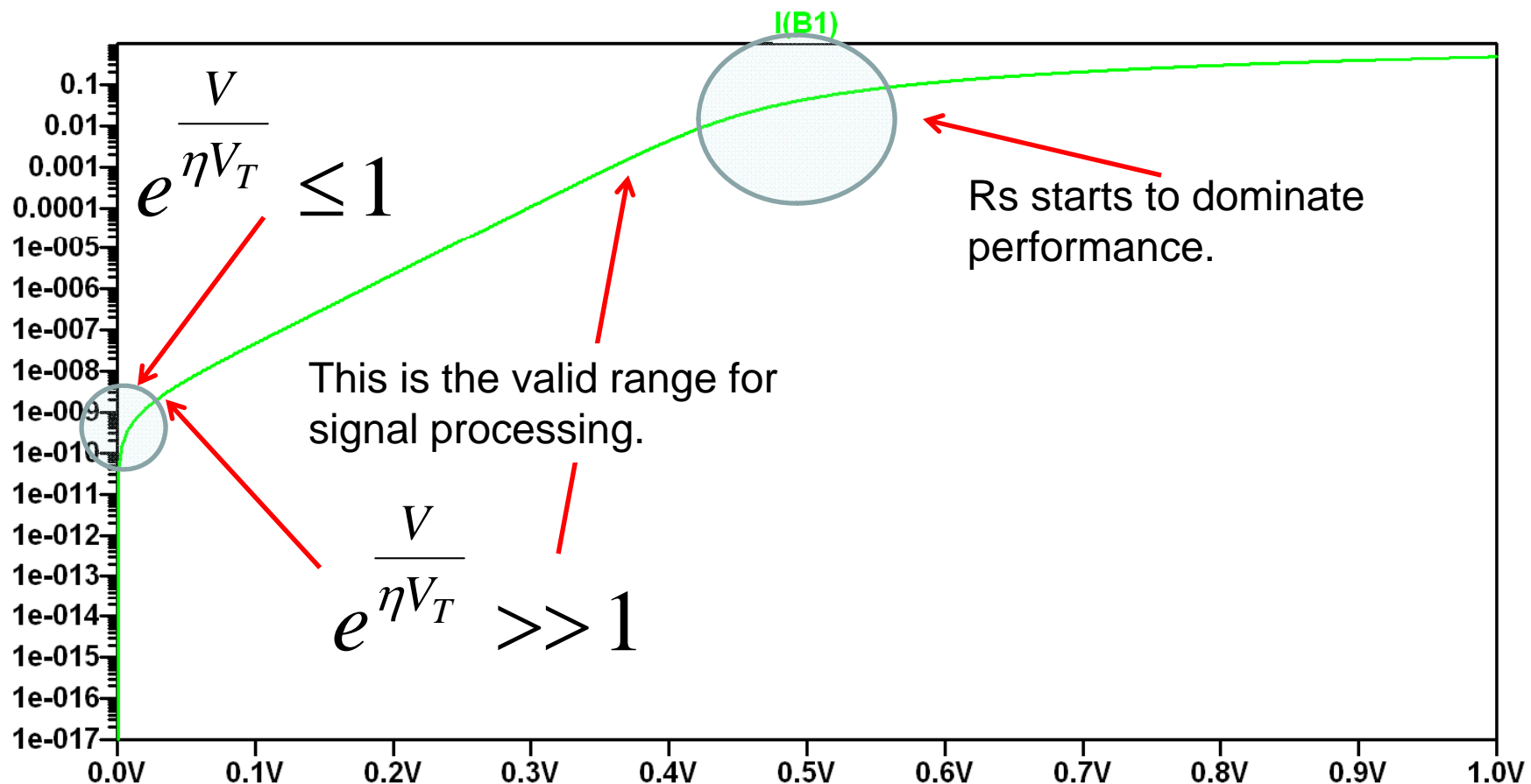

Do not use 10 based log to extract  $I_s$  and  $n$ !!!!

# Extract $I_S$ and $n$ from $\ln(I)$ !

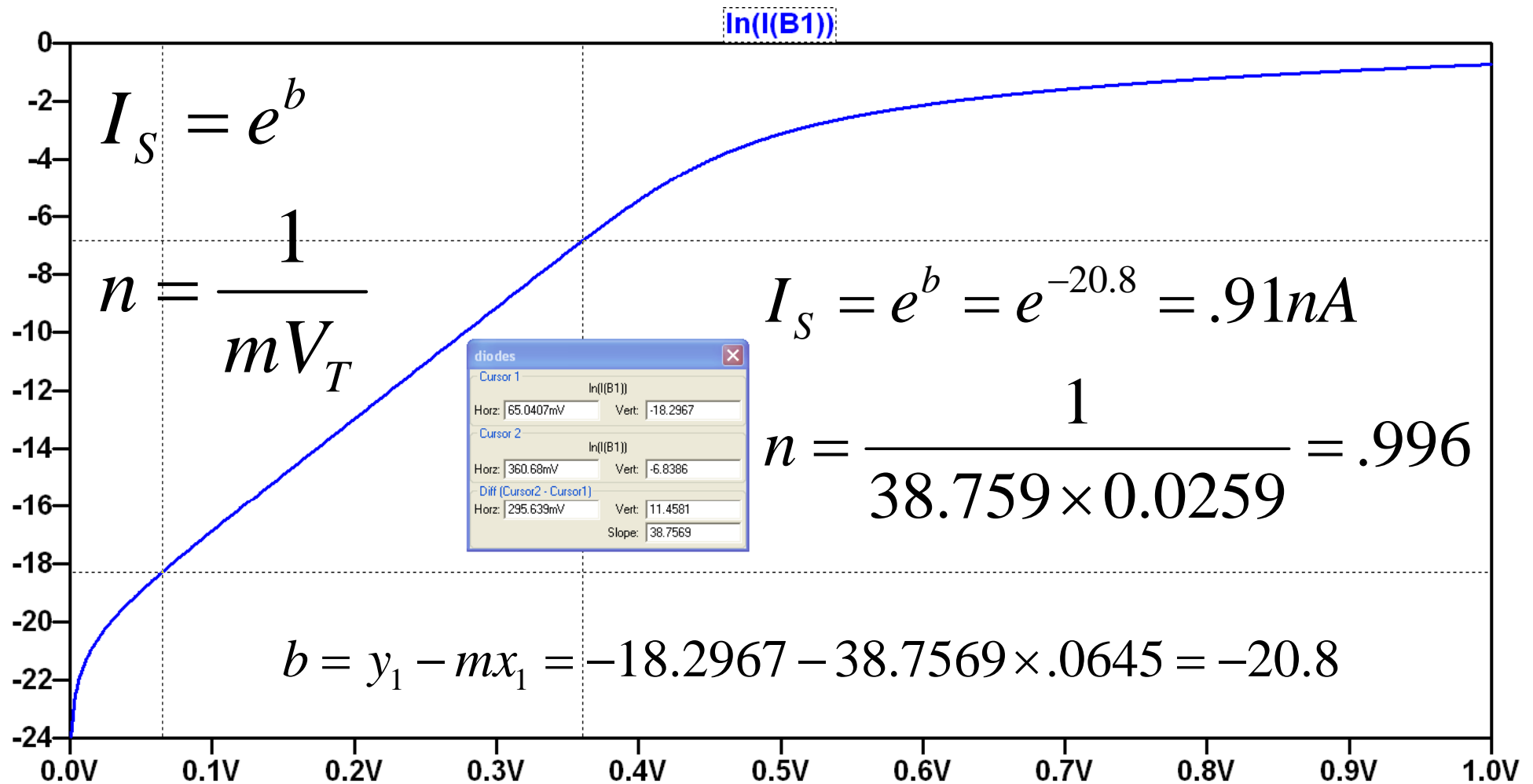

# Replace Set up with “real” diode.

